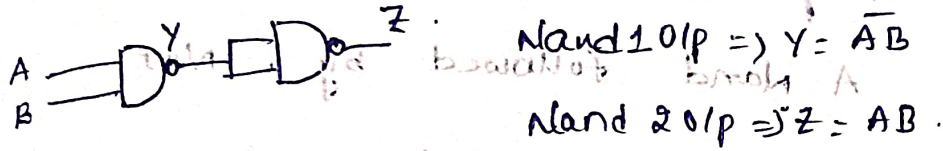


# Assignment - 1

1. Realize all basic gate (AND, OR, NOT) using NAND and NOR separately.


\* Implementation of AND using NAND



1st Nand gate o/p is  $Y = \overline{AB}$

2nd Nand gate i/p is  $Z = \overline{\overline{AB}} \Rightarrow \overline{\overline{A} \overline{B}} \Rightarrow \overline{\overline{A} \overline{B}} = AB$

\* OR gate using NAND

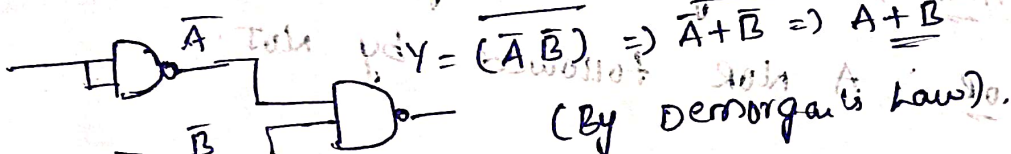


\* NOT using NAND



$A = 0, Y = 1$


$A = 1, Y = 0$

\* AND from NOR

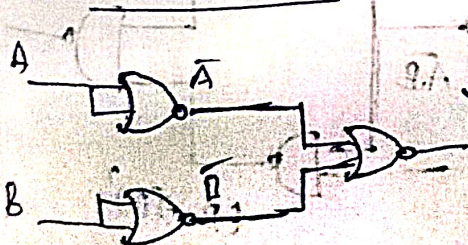

NOR from NOR

\* OR from NOR

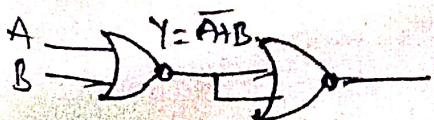

$Z = \overline{\overline{A} + \overline{B}} = AB$



2. Realise all gates using Active Low Inputs?

3. Which gate are called universal gates? Why?

A. NAND

NOT gate :- A NAND gate with both inputs tied together acts as a NOT

AND :- A NAND followed by a NOT

OR :- using De-morgan's law

NOR gate :-

NOT :- Both the inputs are tied together

AND :- using De-morgan's law

OR :- A NOR followed by NOT

4. Give implementation of XOR using minimum number of NAND gates and show the implementation of XOR gate using min no. of NOR gates.

2) XOR using NAND :-

$$F = \bar{A}B + A\bar{B}$$


$$(AB + \bar{A}\bar{B})$$

$$(\bar{A}B + A\bar{B})$$


$$(\bar{A}B)' (A\bar{B})'$$

$$A \cdot \bar{A}B + B \cdot A\bar{B}$$
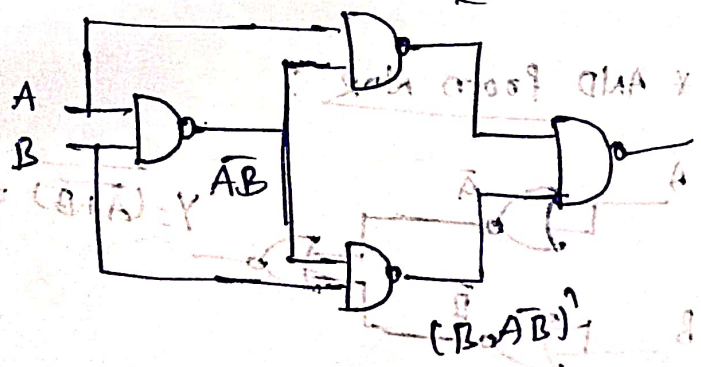
$$[(A \cdot \bar{A}B)' (B \cdot A\bar{B})']'$$





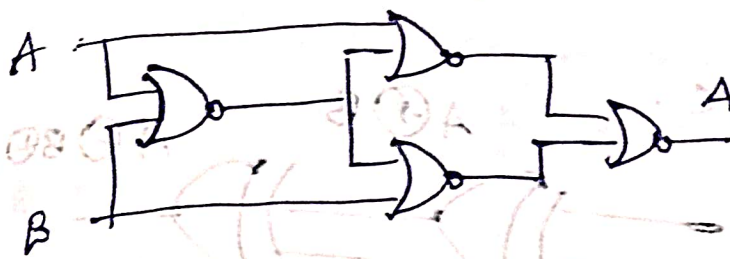

5. Simply  $F = \sum(0, 1, 2, 6, 7, 8, 9, 10, 14, 15)$  in sop & simplify the Boolean exp  $Y = \sum(0, 2, 3, 5, 7, 10, 11, 15)$  in pos by using k-Map.

Sop form :- for eg :

$$A\bar{B} \oplus \bar{A}BC$$

$2^n \rightarrow$  min terms

CD \ AB	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	1	1		1
$\bar{A}B$			1	1
$AB$			1	1
$A\bar{B}$	1	1		1

$$\bar{A}\bar{B} + A\bar{B}$$

$$\bar{A}(\bar{B} + B)$$

$$\bar{A}(\bar{C} + C + D + \bar{D})$$

Pos :  $\pi(0, 2, 3, 5, 7, 10, 11, 15)$

EF \ AD	$\bar{E}\bar{F}$	$\bar{E}F$	$EF$	$E\bar{F}$
$\bar{C}\bar{D}$	0		0	0
$\bar{C}D$		0	0	
$C\bar{D}$			0	
$CD$			0	0

$$(\bar{D} + E)(\bar{E} + F)(\bar{C} + D + F)$$

6. Realise the following using 2 input gate

NAND


a)  $F(A, B, C) = A \oplus B \oplus C$

$A \oplus (B \oplus C)$


$A \oplus (B \oplus C)$



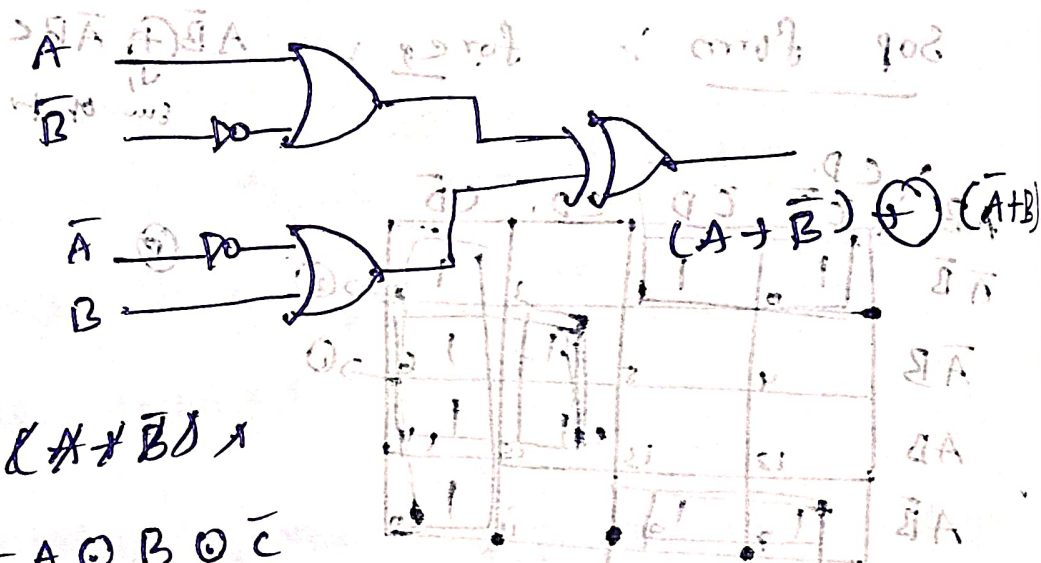b)  $F(A, B) = (A + \bar{B}) \oplus (\bar{A} + B)$



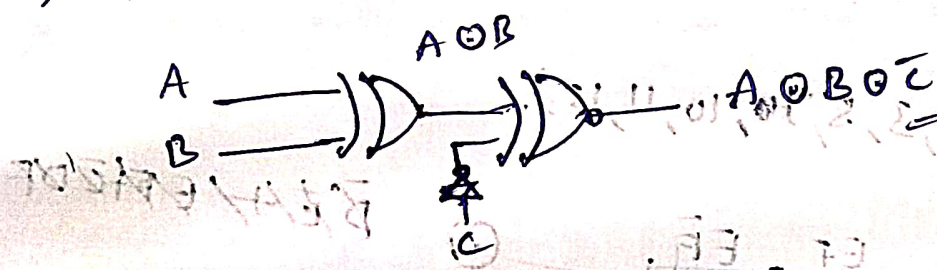c)  $F(A, B, C) = A \odot B \odot \bar{C}$










8. Design BCD to 7 segment display?

Input	a	b	c	d	e	f	g
0 0 0 0	1	1	1	1	1	1	0
0 0 0 1	0	1	1	0	0	0	0
0 0 1 0	1	1	0	1	1	0	1
0 0 1 1	1	1	1	1	0	0	1
0 1 0 0	0	1	1	0	0	1	1
0 1 0 1	1	0	1	1	0	1	1
0 1 1 0	1	0	1	1	1	1	1
0 1 1 1	1	0	1	1	0	0	0
1 0 0 0	1	1	1	1	1	1	1
1 0 0 1	1	1	1	1	0	0	1

Kmap are a, b, c, d, e, f, g

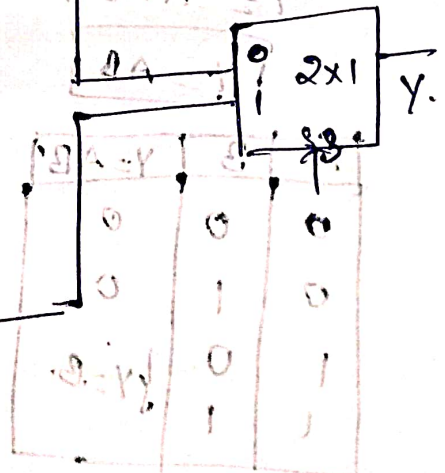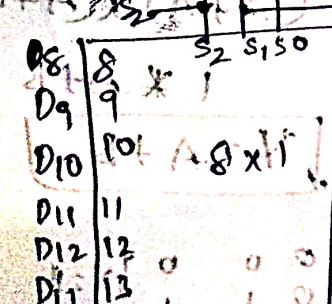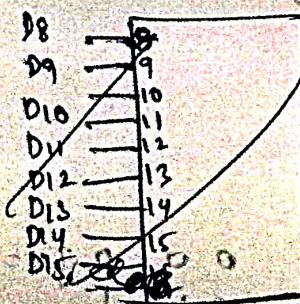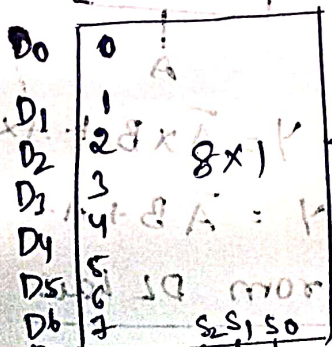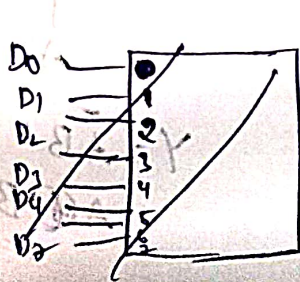
10. Construct 8:1 mux using 2x8:1 & 2:1 mux






9. Design the following gates using min no. of 2:1 mux. a) NOT b) AND c) OR d) XOR

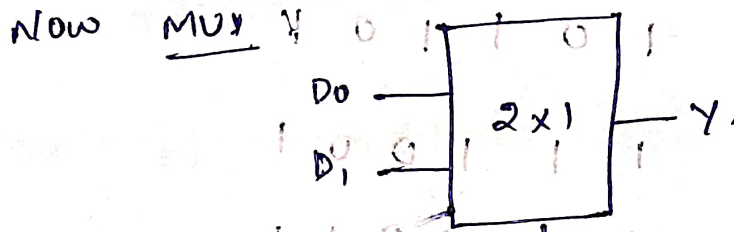a) NOT :-  $A \rightarrow \text{NOT} \rightarrow Y = \bar{A}$



if  $s = 0$ ,  $\bar{s} D_0 + s D_1$   
( $s = 1$ )


now similarly

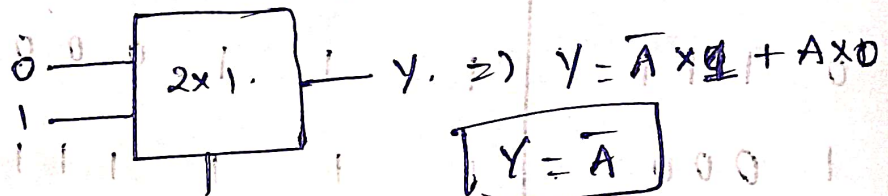

b) AND gate :-

c) OR gate :-


d) XOR gate

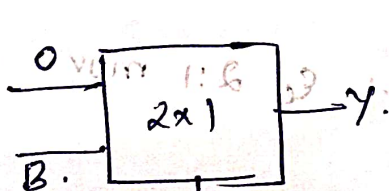

$$Y = \bar{A} \times 0 + AB$$

A	B	$Y = AB$
0	0	0
0	1	0
1	0	0
1	1	1

$Y = B$

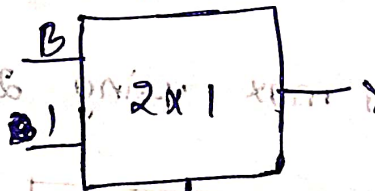

$$Y = \bar{A} \times B + A \times 1$$


$$Y = \bar{A} B + A$$

from DL law:

$$(\bar{A} + A) * (A + B)$$

$$1 * A + B$$

$$Y = A + B$$

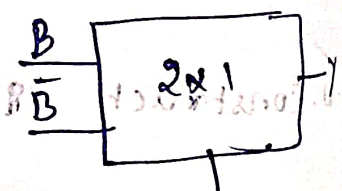

$$Y = \bar{A} B + A \bar{B}$$

$$A \oplus B$$